

Assignment 3, Question 1

Group 24



Gorantla Thoyajakshi - 21CS10026

Ashwin Prasanth - 21CS30009

- We defined a base module called `register` in `Q1_Grp_24_reg.v`, of which we made **8 instances**
 - Each such register has 3 inputs - `LOAD`, `ENABLE` and `in_line` and 1 output - `out_line`
 - Whatever input is fed into the register is done through `in_line`, and the value in the register is read from `out_line`
 - When `LOAD` is high, the register assumes the value in `in_line`
 - When `ENABLE` is high, the value at the register can be obtained at `out_line`, else, `out_line` is at high impedance state
-
- In the top-level module in `Q1_Grp_24_control_reg.v`, we have 6 inputs - `src`, `dest`, `MOVE`, `IN`, `data_in`, `clk` and 1 output - `data_out`
 - `src` and `dest` are 3 bits each, denoting the register number of the source and destination register
 - If `MOVE` is high, the value in `src` register is moved to `dest` register
 - If `IN` is high, the value provided at `data_in` is moved to `dest` register
 - Both cannot be high at the same time, so error is thrown and program is terminated
 - We have made 8 instances of the `register` module, with each of them having their own `LOAD` parameter (in an 8 bit array called `L`), and the same `ENABLE` parameter (`E`) and same input line (`in_line`). Their values are obtained from each of their `out_lines` and stored in an array `R`

- Whenever **MOVE** or **IN** is executed, depending on which register is required, the corresponding **LOAD** value is set to high through **L** and all registers are enabled through **E**. The output, or the value that is moved, is stored in **data_out** (as output). At the end, all **L** and **E** are reset to low
- The whole process is controlled by a clock **clk**

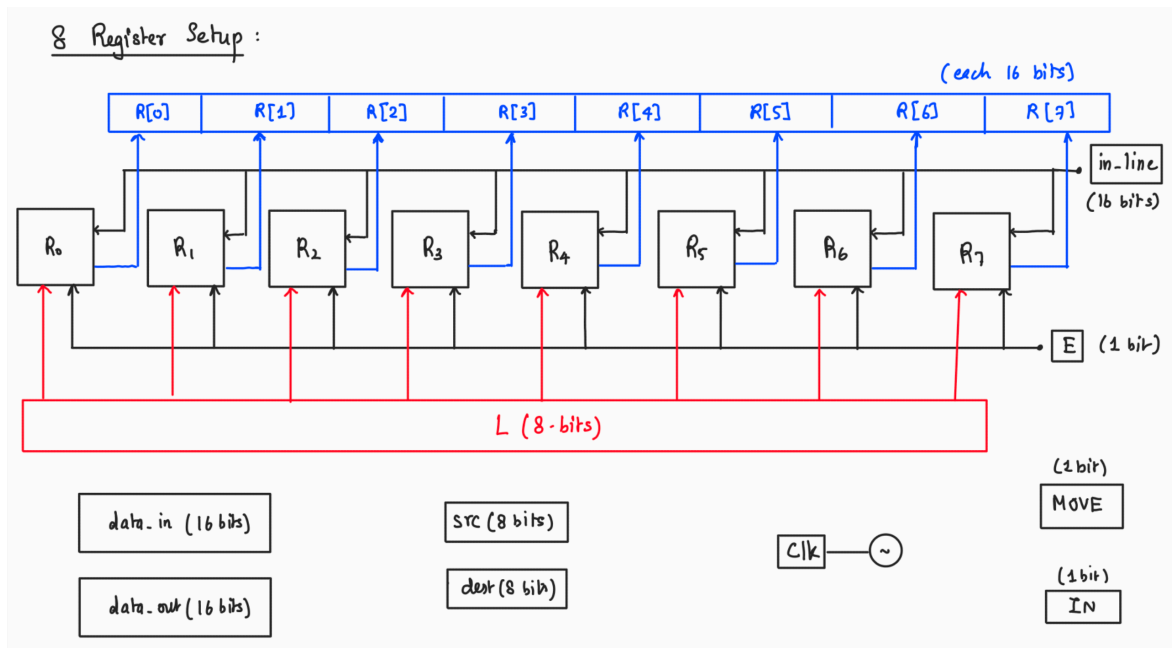 - Here is a simple schematic diagram of the setup:



- There would additionally be some logic involved to access the registers based on **src** and **dest** values, to move the corresponding value from **data_in**, to store the final value in **data_out**, to process whether **MOVE** is to be executed or **IN**, and also to use the **clk** to drive the process
- In the testbench in **Q1_Grp_24_tb.v**, we have tested a few cases of **MOVE** and **IN**, and at the end tested the case of when **MOVE** and **IN** are both set to high (which would throw error)


Assignment 3, Question 2

Group 24

Gorantla Thoyajakshi - 21CS10026

Ashwin Prasanth - 21CS30009

- We have done all the computation in a single module called `gcd`, in `Q2_Grp_24_gcd.v`
- We have 3 inputs `a`, `b`, and `clk`, and one output `result`
- Additional registers `tempa` and `tempb` are used to do operations that will lead to the GCD, and they will have initial values of `a` and `b`
- Whenever the value of `a` or `b` changes (ie, new test case is run), the values of `tempa` and `tempb` are set to the new values of `a` and `b`, and `result` is reset to zero
- `tempa` and `tempb` are iteratively reduced based on whichever is greater, and this is done synchronously with the clock cycle of `clk`, and it is done until one of them assumes the value of zero, in which case the result is the other one.
- Here is a simple schematic diagram of the setup:

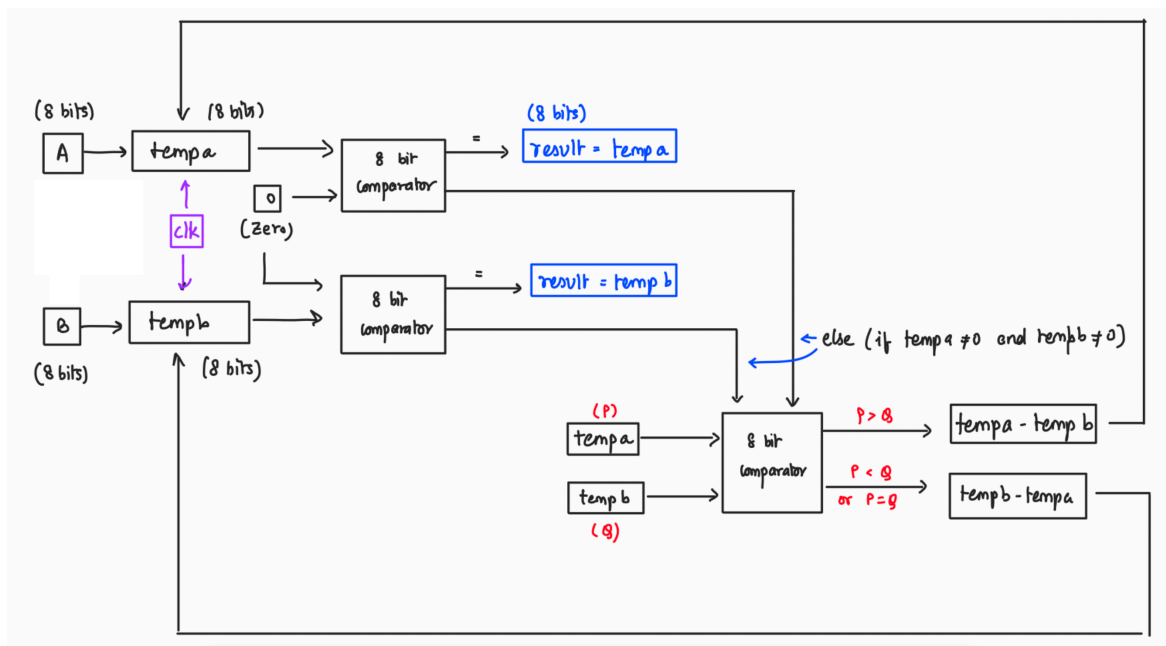

- Additionally there would be some logic involved in assigning the correct value to result, handling the condition when `tempa` and `tempb` are both not equal to zero, finding `tempa-tempb` or `tempb-tempa` (using subtractor module), and using `clk` to drive the process, etc.
- In the testbench in `Q2_Grp_24_tb.v`, we have tested some simple cases of GCD computation, including corner cases like one of them being zero, or both being equal